

LECTURE 140 –ALL DIGITAL FREQUENCY SYNTHESIZER

Objective

- 1.) Demonstrate the application of an ADPLL to a frequency synthesizer suitable for 802.15.4 (Bluetooth/ZigBee)
- 2.) Illustrate the application of 0.18 μ m CMOS to a PLL application

What is Bluetooth/ZigBee?

- A short-range technology for integration into mobile and handheld devices that is target to replace cable connections.
- Specifications:
 - Frequency range: 2400-2483.5 MHz
 - Spectrum spreading: FHSS (Frequency hopping spectrum spreading)
 - $f_k = 2.402 + k$ MHz, $k = 0, 1, \dots, 78$ (dwell time = 0.625ms)
 - Channel bandwidth: 1 MHz
 - Modulation: GFSK (BT = 0.5; $0.28 < h < 0.35$)
 - Receiver sensitivity: -70 dBm @ 0.1% BER
 - Coverage area: Up to 10 m
 - Transmit power: 0dBm (up to 20dBm with power control)



Frequency Synthesizer Specification for 802.15.4 Application


- Frequency range: 2.402 – 2.480 GHz
- Settling time ≤ 220 μ secs
- Phase noise:
 - ≤ -89 dBc/Hz at 0.5 MHz offset
 - ≤ -121 dBc/Hz at 2 MHz offset
- Channel bandwidth: 1 MHz, error tolerance: ± 20 ppm (96 kHz)

Architecture Selection

- Direct digital frequency synthesizer – limited in speed by Nyquist sampling requirements
- Integer-N frequency synthesizer – (channel spacing = reference frequency)
 - Small channel spacing \Rightarrow Large division ratio \Rightarrow Large in-band phase noise
 - Small channel spacing \Rightarrow Small loop bandwidth \Rightarrow Increased switching time
- Fractional-N frequency synthesizer (channel spacing \ll reference frequency)
 - Lower in-band noise
 - Faster locking time
 - Fractional spurs are eliminated by modulating the division ratio using a high-order delta-sigma modulator

System Level Design using Linear Models

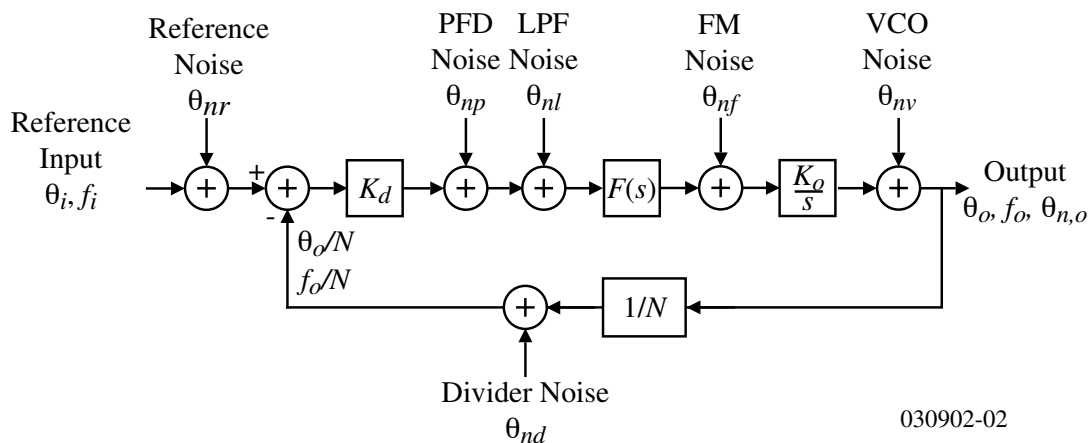- When the PLL is in locked state, the linear model can be used for analysis
 - If the reference frequency \gg loop bandwidth, then we can use the continuous model
- Therefore,



$$B(s) = \frac{\theta_o(s)}{\theta_i(s)} = \frac{G(s)}{1 + G(s)H(s)}$$

where

$$G(s) = \frac{K_d K_o F(s)}{s} \quad \text{and} \quad H(s) = \frac{1}{N}$$

System Level Analysis – Continued

- Output noise power, θ_{no} :


$$\theta_{no}^2 = N^2(\theta_{nr}^2 + \theta_{n,eq}^2) \left(\frac{O(s)}{1 + O(s)} \right)^2 + \theta_{nv}^2 \left(\frac{1}{1 + O(s)} \right)^2$$

where

$$\theta_{n,eq}^2 = \frac{1}{K_d^2}(\theta_{np}^2 + \theta_{nl}^2) = \frac{1}{K_d^2 F(s)^2} \theta_{nf}^2 + \theta_{nd}^2 \quad \text{and} \quad O(s) = \frac{K_d K_o F(s)}{Ns} = \frac{K_v F(s)}{Ns}$$


Note that,
$$\frac{O(s)}{1 + O(s)} = \frac{\frac{K_d K_o F(s)}{N}}{s + \frac{K_d K_o F(s)}{N}} \quad \text{and} \quad \frac{1}{1 + O(s)} = \frac{s}{s + \frac{K_d K_o F(s)}{N}}$$

 - Reference noise and the VCO inherent noise are the two major sources of phase noise in a PLL. This is illustrated below as,




Direct Digital Frequency Synthesizer

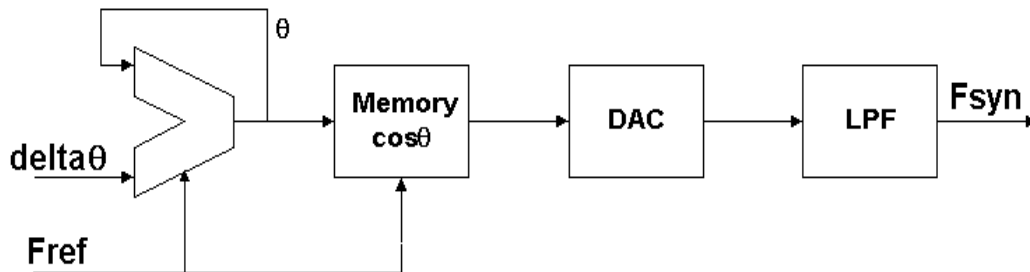- Direct digital frequency synthesizer (DDFS)
 - Advantage: High frequency resolution, fast switching time
 - Disadvantage: High power consumption, limitation of the highest frequency by the Nyquist sampling theorem, discrete narrow band spurious signals
- The DDFS methods are combined with PLLs to achieve fine frequency steps with reasonable phase noise.



PLL Based Frequency Synthesizer


- PLL is a negative feedback system whose output frequency is locked onto an input signal.
 - Phase detector is the error amplifier
 - Lowpass filter suppresses the high frequency components of the phase detector
 - VCO
- Low cost and good spurious suppression
- Coarse frequency resolution or frequency steps and poor phase noise
- Slow switching speed for negative feedback loop
- Closed-loop transfer function:

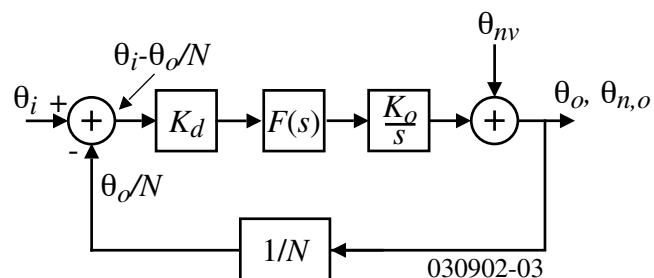

$$B(s) = \frac{\theta_o(s)}{\theta_i(s)} = \frac{G(s)}{1 + G(s)H(s)} = \frac{\frac{K_d K_o F(s)}{s}}{1 + \frac{K_d K_o F(s)}{N s}} = \frac{N \omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$


Charge Pump Frequency Synthesizer

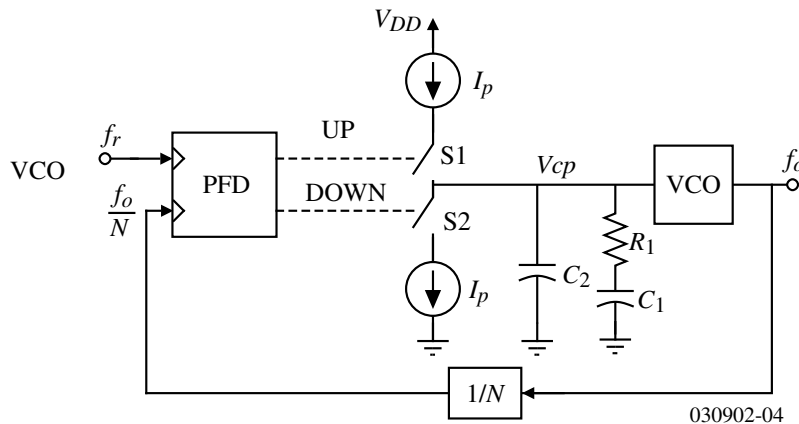- Charge pump phase locked loop (Type II, 3rd order PLL)
 - Advantage: Low phase noise
 - Disadvantages: Process dependent, slow locking speed, large passive external elements (R s and C s)




Integer-N Frequency Synthesizer

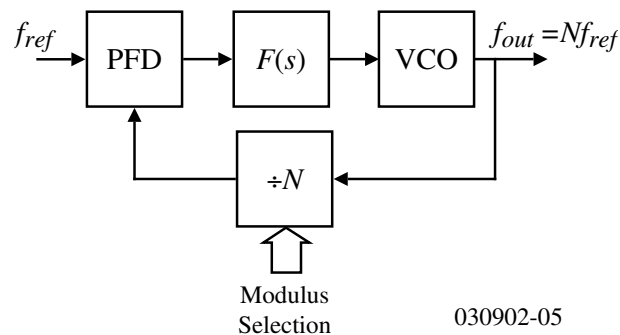- Integer-N frequency synthesizer:
 - $f_o = Nf_{ref}$, N = integer number
 - Inverse relationship between step size and phase noise
 - To achieve small channel spacing, a low f_{ref} is required which means a narrow loop bandwidth resulting in increased settling time and reduced VCO noise suppression
 - Low f_{ref} means a large integer N , resulting in increased in-band phase noise



Dual Loop Frequency Synthesizer

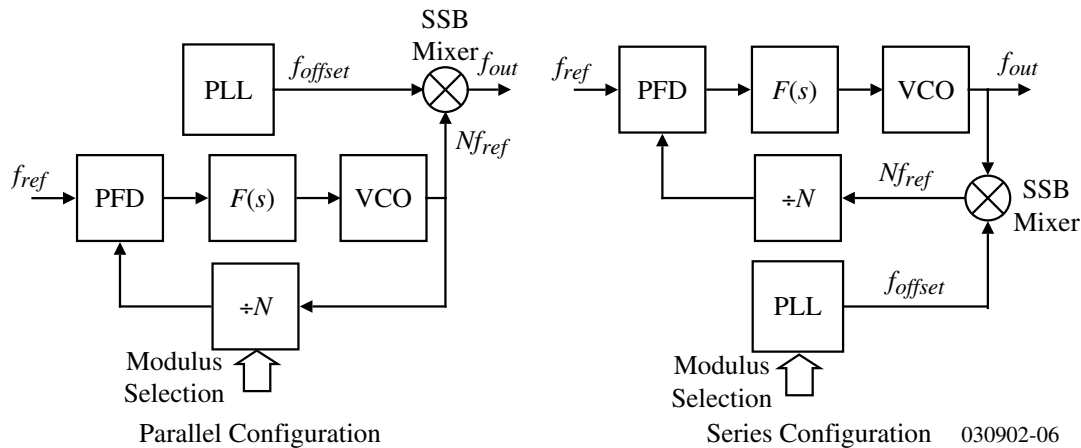- Dual loop frequency synthesizer:
 - Mixer is incorporated into the PLL altering the relationship between the channel spacing and the reference frequency of the integer N synthesizer
 - 2 dual loop types: A combination of 2 PLLs by a single sideband mixer in parallel and in series
 - Adds a fixed high offset frequency and a low variable frequency



Dual Loop Frequency Synthesizers - Continued

- Architectural comments:
 - Parallel configuration: A fixed frequency + varying frequency. Gives large spurs at the output
 - Series configuration: Varying frequency is added inside the loop resulting in a larger settling time and a small sideband from the mixer
 - The loop bandwidth of the high frequency loop can be large which gives more reduction of phase noise close to the carrier
 - The frequency division of the divider can be reduced with the fixed offset frequency
 - Sidebands are produced from the non-ideal SSB mixing and larger power consumption is required

Fractional-N Frequency Synthesizer

- Fractional-N frequency synthesizer:


- Doesn't require more current, complexity or bigger area

- $f_{ref} \gg f_{step}$

- $f_o = f_{ref} \left(N + \frac{K}{F} \right)$

$N_{fractional}$: (Divide by $N+1$ every K VCO cycles out of F cycles and by N for the remaining cycles)
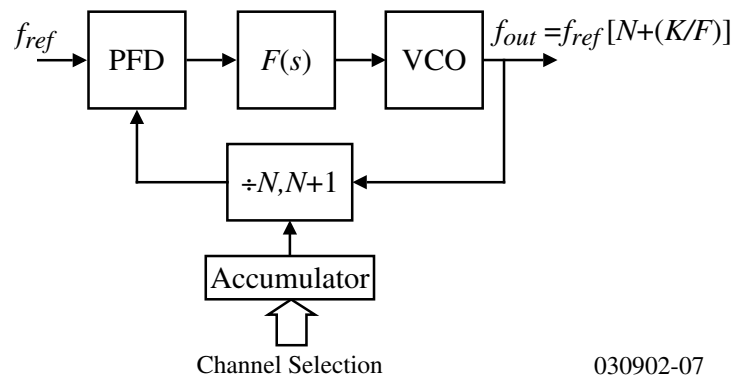
$$\therefore N_{fractional} = (N+1) \frac{K}{F} + N \left(1 - \frac{K}{F} \right) = N + \frac{K}{F}, \text{ where } K \geq 0$$



030902-07

All-Digital Frequency Synthesizer

- Apply digital filter to achieve a single-chip frequency synthesizer

- Fully integrated frequency synthesizer

- Easy to implement for a multi-mode application (i.e. W-CDMA/GPRS/GSM)

- Increase design robustness

- Apply MASH delta-sigma modulator

- Reduced spurs

- Fast locking time


- Use a switched-current oscillator

- Wide locking range

- Fast locking time

All Digital Frequency Synthesizer – Continued


Block diagram:

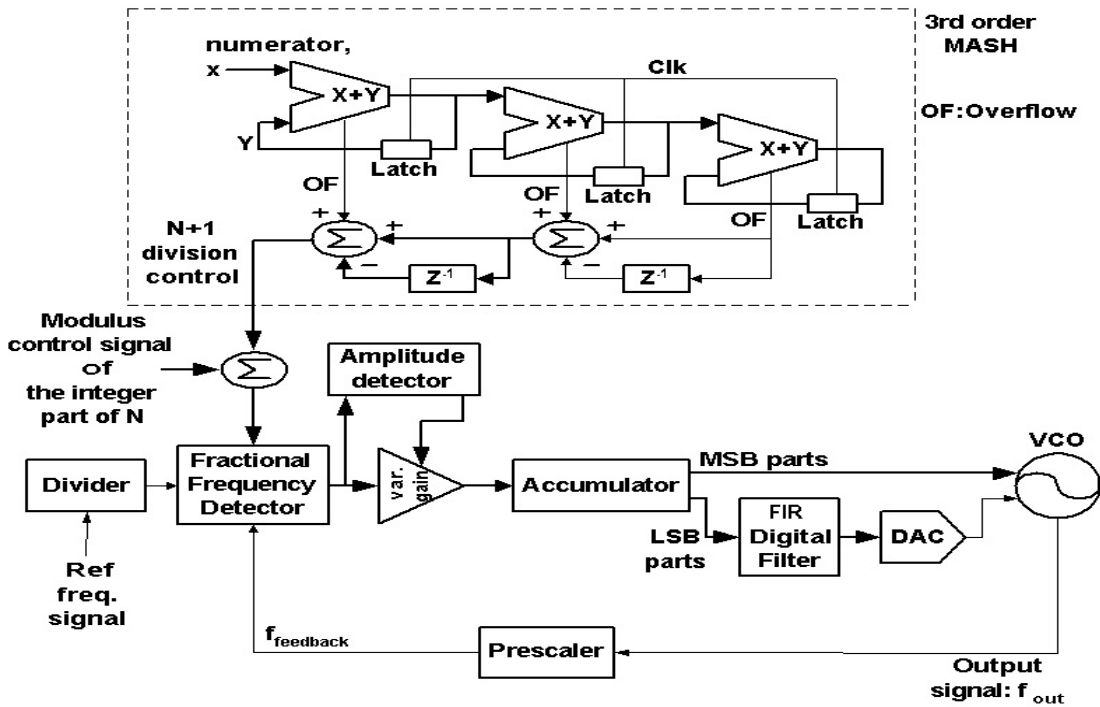

CMOS Phase Locked Loops

© P.E. Allen - 2003

 Linear Model of the ADPLL Frequency Synthesizer





$$H(z) = \frac{\omega_{feedback}}{\omega_{ref}} = \frac{KF(z)z^{-1}}{1 - z^{-1}[1 - KF(z)]}$$



where

$$K = \frac{K_{da}K_{vco}K_a}{\omega_{ref}}$$

  System Level Unit Step Response and Pole-Zero Plot



  
System Level Locking Time Simulation (Bluetooth)




CMOS Phase Locked Loops

© P.E. Allen - 2003

 System Level Phase Noise Simulation (Bluetooth)


 
$$\text{Fractional} = \frac{\text{Numerator}}{\text{Denominator}} = \frac{32}{64}$$




$$\text{Fractional} = \frac{\text{Numerator}}{\text{Denominator}} = \frac{0}{64}$$

Block Design – Third-Order $\Delta\Sigma$ Modulator

- Used to eliminate the fractional spurs by modulating the division ratio
- A third-order modulator is used to meet the higher spurs specification

A first-order $\Delta\Sigma$ modulator:

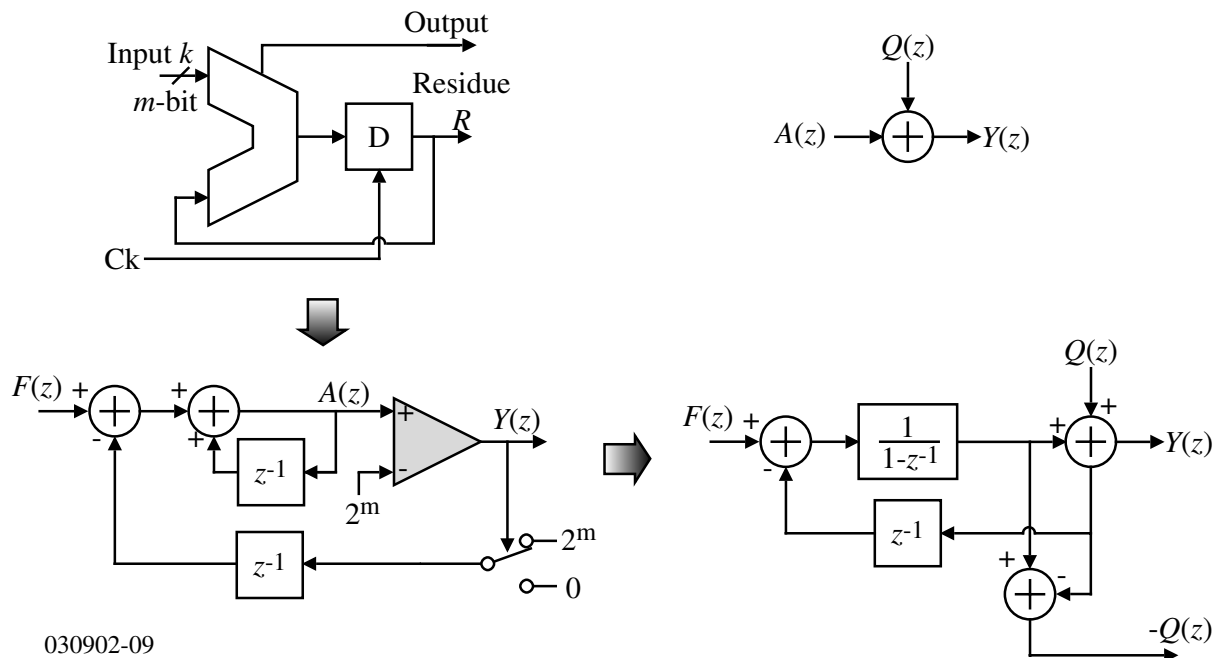


030902-09


Block Design – Third-Order $\Delta\Sigma$ Modulator – Continued

Third-order MASH block diagram and simulation:
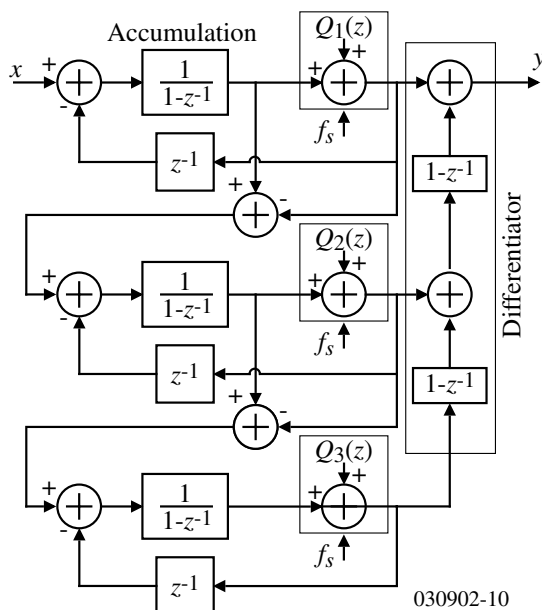
$$y(z) = x(z) + (1 - z^{-1})^3 q_3(z) = x(z) + H_{\text{noise}}(z) q_3(z)$$




030902-10

 

Block Design – Continued

Logic design:

 - Conventional CMOS static logic
 - Wide noise margins
 - High packaging density
 - Zero static power dissipation
 - Coupling between the analog blocks and the digital blocks
 - Susceptible to power supply noise
- Current Mode Logic
 - Constant current source
 - Differential input and output



Block Design – Continued


8-bit DAC:

- Symmetric 2-stage current cell matrix architecture
- A 4-bit MSB current cell matrix and a 4-bit LSB current cell matrix
- Uses thermometer code
- Monotonic conversion characteristic

$$I_{out} = I_{MSB}(2^3B_7 + 2^2B_6 + 2^1B_5 + 2^0B_4) + I_{LSB}(2^3B_3 + 2^2B_2 + 2^1B_1 + 2^0B_0)$$



$$I_{MSB} = 16 I_{LSB}$$

$$V_{out} = I_{out} R_{Load}$$

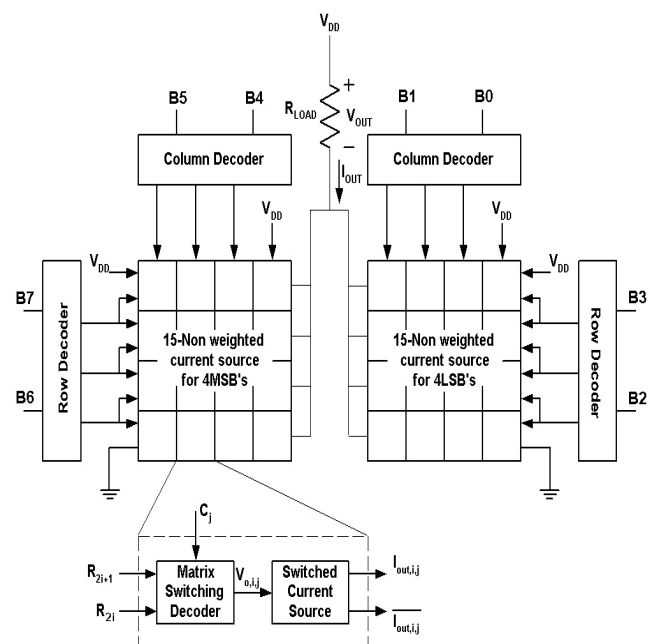

Prescaler:

  - Issues – high operating frequency, low power dissipation, low phase-noise
- Conventional Current Mode Logic (CML):



- Feedback CML (Transistors MF₁ and MF₂)

$$A(j\omega) = \frac{A_d(j\omega)}{1 + F_b A_d(j\omega)}$$

$$= \frac{A_d(0)}{1 + F_b A_d(0)} = \frac{1}{1 - j\left(\frac{\omega}{\omega_p}\right)\left(\frac{1}{1 + F_b A_d(0)}\right)}$$


where

F_h = the gain of the feedback transistors

The bandwidth of the feedback CML \gg the bandwidth of the conventional CML.

Block Design – Continued


Feedback CML D Flip-flop implementation:

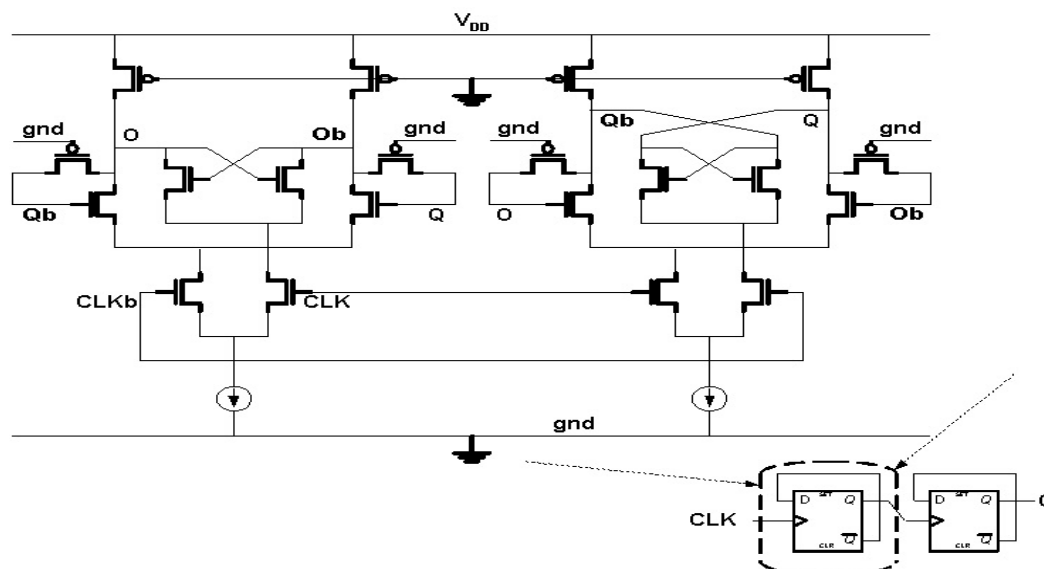


Block Design – Continued

FIR Digital Filter:

(a.) Single flow graph of n th order

 

(b.) Linear phase transpose direct form.

 

Experimental Results

(In progress)